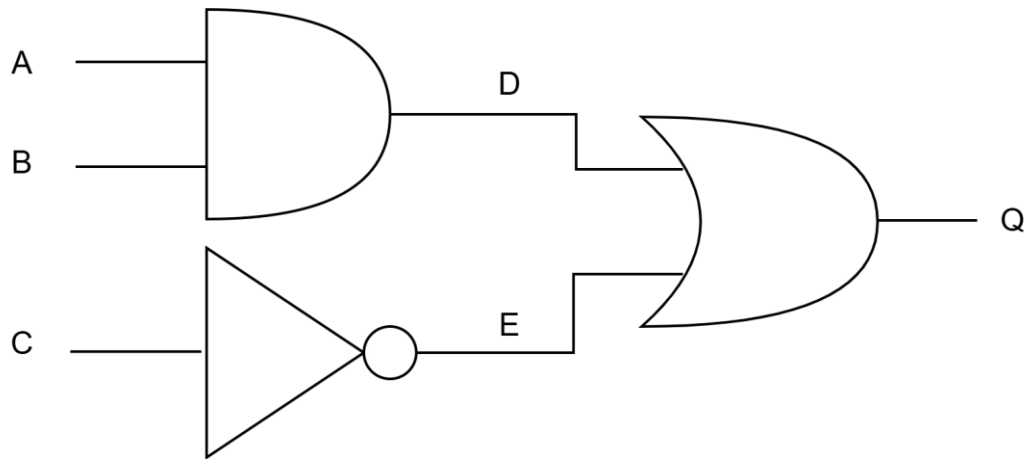


1. Create a truth table for the logic gate above.


A	B	C	D	E	Q

2. Write the logic equation for the logic gate above



3. Create the truth table for the logic gate above.

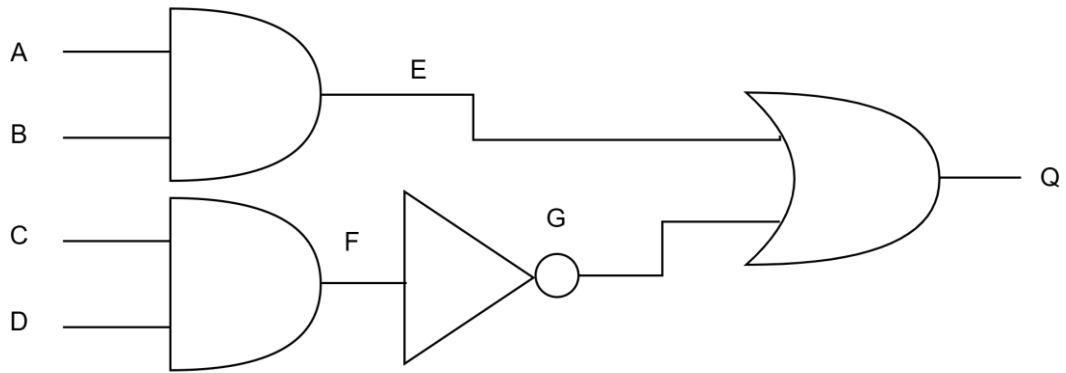4. Write the logic equation for the logic gate above




5. Complete the following truth table.

A	B	C	D	E	F	G	Q
			0				
			1				
			0				
			1				
			0				
			1				
			0				
			1				
			0				
			1				
			0				
			1				
			0				
			1				
			0				
			1				

6. Write the logic equation for the logic gate above

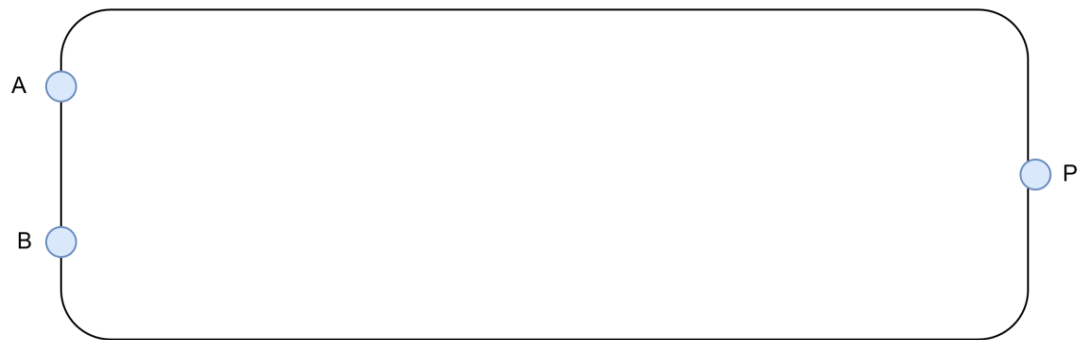7. Draw the logic diagram for the following logic equation

$$P = ((\text{NOT } B) \text{ AND } (A \text{ AND } B))$$



8. Draw the truth table for the above logic equation

A	B			P